

Conventional Latch Type Sense Amplifier(Mux16 configuration)

ECE-611 (Memory Design and Test)

Abhishek Bidhan MT21151

Nikhil Pratap Singh MT21199

Sudhanshu Trivedi MT21212



INDRAPRASTHA INSTITUTE *of*
INFORMATION TECHNOLOGY
DELHI



Problem Statement





Design of Conventional latch-type sense amplifier (for MUX-16 configuration) with the following conditions:


- ◆ Voffset at 3-sigma = 25mV (after layout extraction) @wc, 1.08V
- ◆ SA-enable to Qlatch delay = 200ps @wc, 1.08V
- ◆ SA-enable pulse width = 100ps @wc, 1.08V
- ◆ Study incremental benefit of Common Centroid Layout
- ◆ Study incremental benefit of Structural Matching

In this, we have to design a latch-type sense amplifier circuit with a pre-charge circuit and latch circuit, where the two inputs to the sense amplifier are BL and BLB from the memory cell. We have to minimize offset voltage below 25 mv (After layout extraction). For this design, we will be using the common centroid layout in order to have a common V_t for pull-down devices in the circuit.


Design Schematic

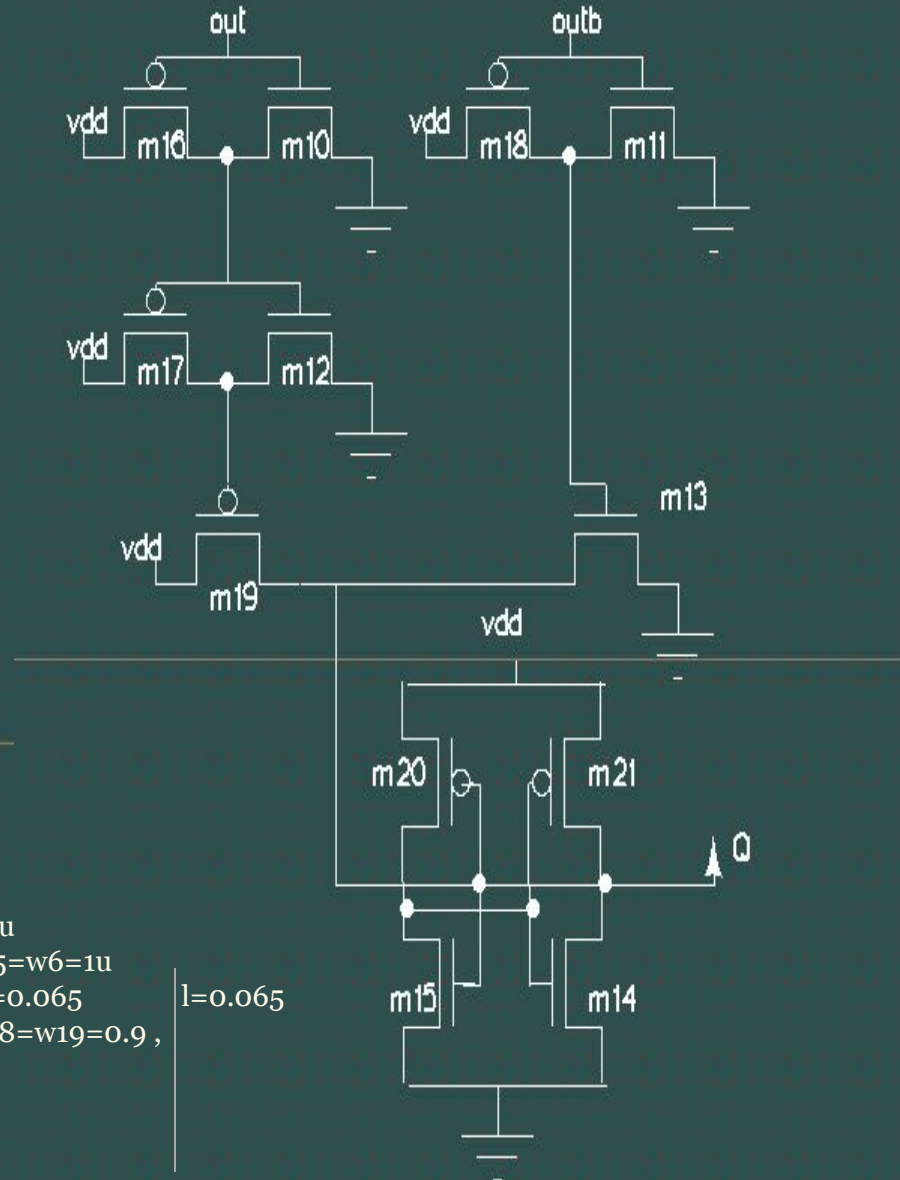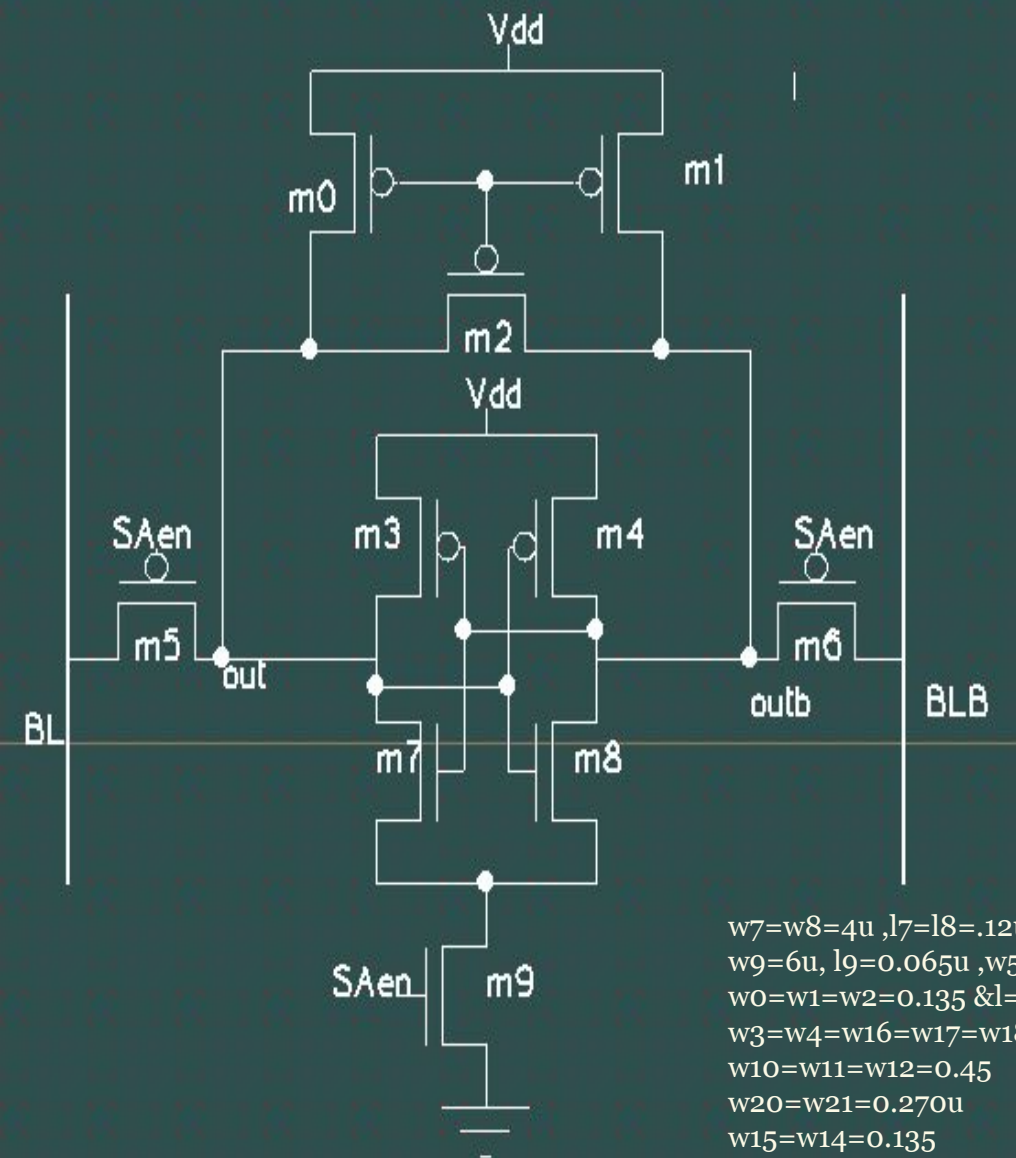

Read-0 (Functionality)

 


Read-0 (Delay)

 


CASE	PVT	DELAY
Worst Case	SS, -40	104.29 ps
Best Case	FF, -40	52.86 ps

Read-0 (Offset)

 


Voffset = 18.72 mV (at worst PVT → FF, -40)

Read-1 (Functionality)

 


Read-1 (Delay)

 


CASE	PVT	DELAY
Worst Case	SS, -40	121.31 ps
Best Case	FF, -40	67.95 ps

Read-1 (Offset)

 


Voffset = 20.59 mV (at worst PVT → FF, -40)

Layout (Common Centroid part)

 


Here we have used common centroid layout for the 2 differential pull down nMOSs (M7 and M8), as we want very least V_t variations in those 2 devices due to Process variations.)

Layout (With PP – NP layers)

 

Width → 9.575 μm , Height → 7.84 μm , Total Area → 75.06 μm^2

Layout (Without NP-PP layers)

 

Challenges



- ◆ Challenges are there to minimize Voffset
- ◆ Finding the Footer and pull down size to maintain 3sigma offset
- ◆ And reducing SAen to Qlatch delay below 200 ps, with proper sizing
- ◆ Proper matching of pull down devices , it was mitigated with common centroid approach in layout
- ◆ Utilizing area while layout making



◆ Technical Conclusions

✿ What worked?

We have designed the layout with common centroid technique and maintained symmetry in layout

✿ What did not work?

Layout can be more compact with utilization of available area

◆ Emphasise on learning from the project

✿ Common centroid layout , collaboration with others teams and their design

✿ Better understanding of topics

◆ Future plans

✿ We will also try to generate the Pre-charge signal from the clock instead of directly using it as separate signal.

✿ We will try to extend and design complete I/O circuitry by ourself.

Some references that we have followed

- [A High Speed Low Voltage Latch Type Sense](#)
- [Comparative analysis of Sense Amplifiers for SRAM in 65nm CMOS technology](#)
- MDT and DVD classroom lectures.

